

Experiment no: 06

Jannatul Ferdous Binta Kalam Priyo

Name of the Experiment: Determination of the ratio of the electromotive forces of two cells by using potentiometre


Questions on theory (all diagrams should be drawn by using a pencil and a scale)

*1) What is electromotive force of a cell? [0.25]

Ans: Electromotive force of a cell is the amount of work performed by the cell to move 1 unit of positive charge (1C), starting from a point of a circuit, through the whole circuit, and then bring it back to the starting point.

*2) See Figure 1. Draw it and work out the rule of voltage division for this circuit. [0.25]

Ans:

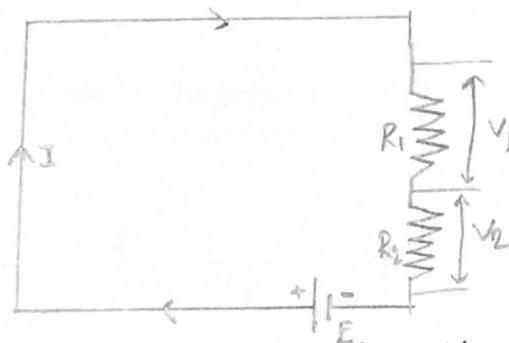

According to Ohm's law, $V_1 = IR_1$

$$V_2 = IR_2$$

$$\therefore E = V_1 + V_2$$

$$= IR_1 + IR_2$$


$$= I(R_1 + R_2)$$

$$\therefore I = \frac{E}{R_1 + R_2}$$

$$\text{For } V_1 = \frac{R_1}{R_1 + R_2} (E)$$

$$V_2 = \frac{R_2}{R_1 + R_2} (E)$$

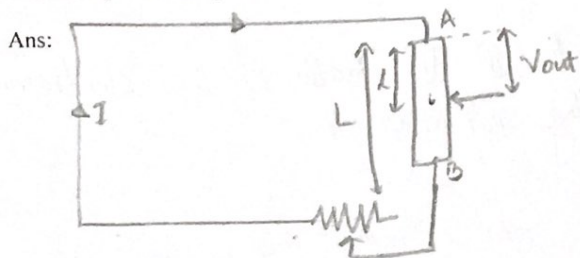*3) See Figure 2. Draw it and work out an expression of V_{out} in terms of E, l, L, R, R_h and σ . σ is the resistance per unit length of the conductor AB. R is the total resistance of the conductor. [1]



Total resistance of the conductor

$$R = R_{AJ} + R_{JB}$$

If σ is the resistance per unit length of the conductor then

$$R_{AJ} = l\sigma \text{ and } R = L\sigma$$

According to potential divider rule:

$$V_{out} = \frac{R_{AJ}}{R_{AJ} + R_{JB}} (E)$$


$$= \frac{R_{AJ}}{R + R_h} E$$

$$= \frac{l\sigma}{L\sigma + R_h} E$$

$$\therefore V_{out} = \frac{E}{L + \frac{R_h}{\sigma}} l$$

*4) See Figure 3. Draw it and work out an expression of the current passing through the galvanometer, I_G as shown in equation (6). [2]

Ans:

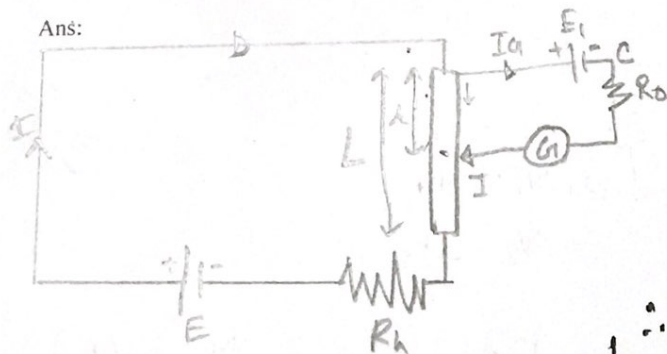

According to Ohm's law,

$$V_e - V_i = I_G R_0$$

Voltage difference across E_1 ,

$$V_A - V_B = E$$

$$\therefore V_A - V_B = E_1 + I_G R_0$$

$$\therefore \frac{El}{L + \frac{R_h}{\sigma}} = E_1 + I_G R_0$$

$$\Rightarrow \frac{El}{L + \frac{R_h}{\sigma}} - E_1 = I_G R_0$$

$$\therefore I_G = \frac{1}{R_0} \left[\frac{El}{L + \frac{R_h}{\sigma}} - E_1 \right]$$

*5) When I_G is zero, then σ

Ans: $\frac{R_h}{\sigma}$

*5) When I_G is zero, then show that, $E_1 = \frac{E}{L + R_h/\sigma} l$ [0.25]

$$\text{Ans: } I_G = \frac{1}{R_0} \left[\frac{E l}{L + R_h/\sigma} - E_1 \right] \quad \left| \quad \therefore E_1 = \frac{E l}{L + R_h/\sigma} \right.$$

if, $I_G = 0$


$$\frac{1}{R_0} \left[\frac{E l}{L + R_h/\sigma} - E_1 \right] = 0$$

*6) If l_1 and l_2 are the length of the segment of the potentiometer's wire and the null point, correspond to E_1 and E_2 , then show that $\frac{E_1}{E_2} = \frac{l_1}{l_2}$ [0.25]

$$\text{Ans: For } l_1, E_1 = \frac{E l_1}{L + R_h/\sigma} \text{ --- (i)} \quad \left| \quad \begin{array}{l} \text{(i)} \div \text{(ii)} \\ \frac{E_1}{E_2} = \frac{l_1}{l_2} \end{array} \right.$$

$$\text{For } l_2, E_2 = \frac{E l_2}{L + R_h/\sigma} \text{ --- (ii)}$$

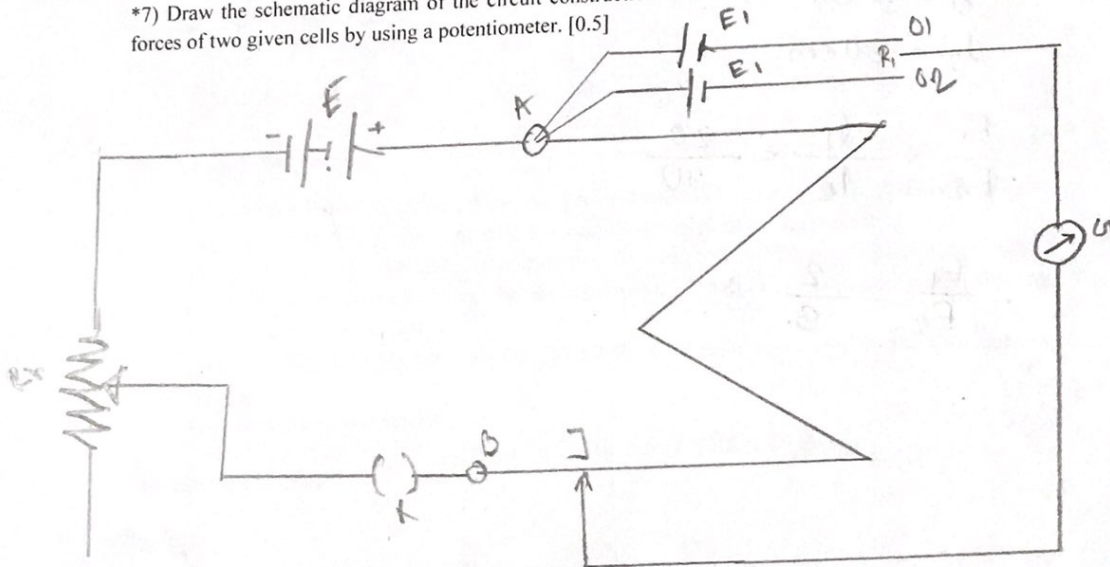*7) Draw the schematic diagram of the circuit construction to determine the ratio of the electromotive forces of two given cells by using a potentiometer. [0.5]



- 8) See the Figure 5 which shows the circuit construction to compare the emf of two cells with a potentiometer. When OO_1 is connected then the null point of the galvanometer is found at J_1 . When OO_2 is connected then the null point of the galvanometer is found at J_2 . What is the approximate value of $\frac{E_1}{E_2}$?
- [0.5]

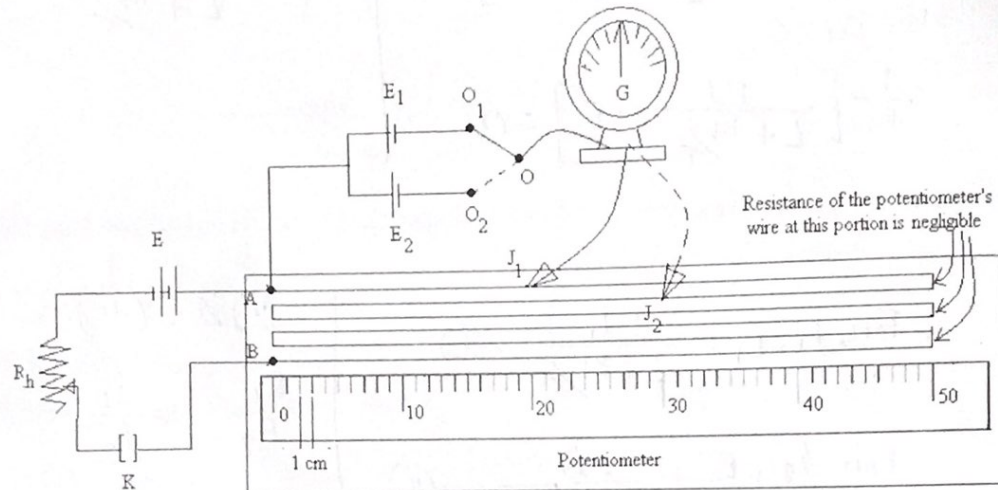


Figure 5: Figure for question 8

Ans:

$$l_1 = 20 \text{ cm}$$

$$l_2 = 30 \text{ cm}$$

$$\frac{E_1}{E_2} = \frac{l_1}{l_2} = \frac{20}{30}$$

$$\therefore \frac{E_1}{E_2} = \frac{2}{3}$$

- Draw the data table(s) and write down the variables to be measured shown below (in the 'Data' section), using pencil and ruler BEFORE you go to the lab class.
- Write down your NAME and ID on the top of the page.
- This part should be separated from your Answers of "Questions on Theory" part.
- Keep it with yourself after coming to the lab.

Data

Table: Data for calculating the ratio of emf of two cells

No. of obs.	Cell	Null points			Total length (cm)	$E_1/E_2 = l_1/l_2$	Mean E_1/E_2
		Wire - segment number	Scale reading (cm)	Mean scale reading (cm)			
1	First (E_1)	8	79.5	700	779.5	0.996	0.996
	Second (E_2)	8	82	700	782		
2	First (E_1)	9	85	800	885	0.997	
	Second (E_2)	9	87.5	800	887.5		
3	First (E_1)	10	69	900	969	0.996	
	Second (E_2)	10	72	900	972		
4	First (E_1)	6	86	500	586	0.996	
	Second (E_2)	6	88	500	588		
etc.							

- READ the PROCEDURE carefully and perform the experiment by YOURSELVES. If you need help to understand any specific point draw attention of the instructors.
- DO NOT PLAGIARIZE data from other group and/or DO NOT hand in your data to other group. It will bring ZERO mark in this experiment. Repetition of such activities will bring zero mark for the whole lab.
- Perform calculations by following the PROCEDURE. Show every step in the Calculations section.
- Write down the final result(s)

Calculations Mean, $\frac{E_1}{E_2} = \frac{0.996 + 0.997 + 0.996 + 0.996}{4} = 0.996$

Results :

The ratio of electromotive force of two cell is 0.996.

Questions for Discussions


- 1) If you see the galvanometer's pointer always deflects towards same direction when you make the contact between the jockey and the wire, near end A and end B; what might be the possible reason(s) for this? [0.5]

Ans: When I make the contact between the jockey and the wire near end A and end B, the possible reason might be high resistance of rheostat if the resistance of rheostat increase a lot then the galvanometer point always deflects to the same direction as wire and jockey.


- 2) We can use a voltmeter or a multi-meter to measure the emf of a cell. What might be a drawback of using a voltmeter or a multi-meter for this purpose? How can a potentiometer be useful to avoid this drawback? [0.5]

Ans: Using a voltmeter or multimeter the draw back may be the internal resistance which can give inaccurate measure of emf of a cell. But potentiometer can be useful to avoid this draw back. Potentiometer has not any internal resistance. That's why we can get accurate measure of emf of a cell.

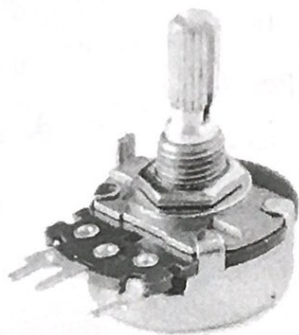- 3) The Figure 6 shows a typical single turn potentiometer, but its structure is quite different from the potentiometer which you have used in the lab. You can see three terminals, and a knob which can be rotated. In the right side, you see its internal structure. The grey colored circular object is a conductor of significant resistance having uniform thickness. Yellow colored object is a good conductor whose resistance can be neglected, an L shaped portion of which touches the circular portion around the circular conductor a point J as shown in the Figure 6. By rotating the knob we can slide this L shaped portion around the circular conductor. Explain how you can use this single turn potentiometer as a potential divider. [1]



(a) External view

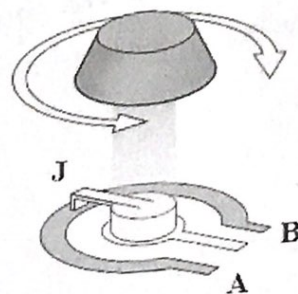

(b) Internal structure

Figure 6: Single turn potentiometer (Courtesy: Wikimedia)

Ans: In fig (b) we can connect the A and B points like a potentiometer. So, point A is connected to main cell E while point B is connected to switch K. The knob J is used as a Jockey and rotating it we can get an output voltage difference V_{out} between point A and J. If the distance between A and J increases V_{out} increases. In this way we can use a single turn potentiometer as a potential divider.